

<b>Course Name:</b>	Elements of Electrical and Electronics Engineering	<b>Semester:</b>	I
<b>Date of Performance:</b>	/ / 2023	<b>Batch No:</b>	C5_3
<b>Faculty Name:</b>		<b>Roll No:</b>	16010123325 (53)
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	/ 25

## Experiment No: 5

### Title: Maximum Power Transfer Theorem

#### Aim and Objective of the Experiment:


- To observe maximum power transfer across load resistor in a D.C circuit.

#### COs to be achieved:

**CO1:** Analyze resistive networks excited by DC sources using various network theorems.
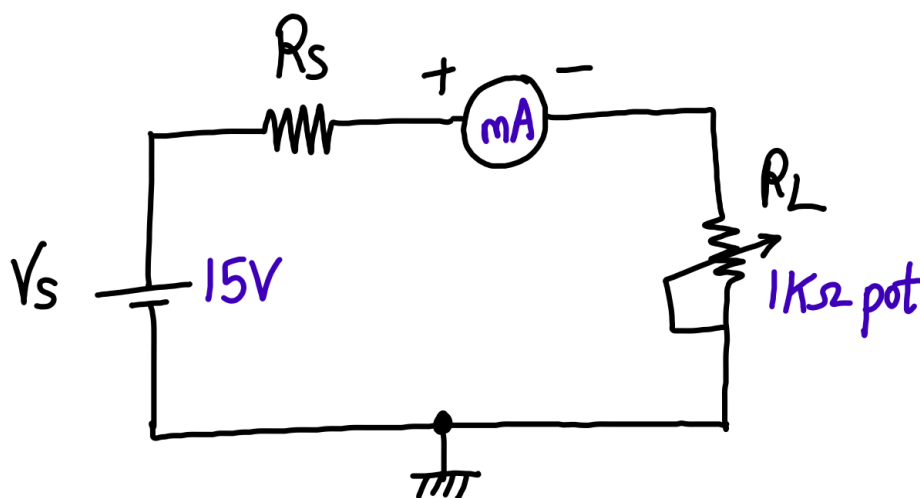
#### Circuit Diagram:

$V_s = 15\text{ V}$  and  $R_s = 560\ \Omega$




### Stepwise-Procedure:

1. Set D.C. supply voltage  $V_S = 15\text{ V}$
2. Vary  $R_L$  in the range  $100\ \Omega$  -  $1\text{ K}\Omega$  in steps of  $100\ \Omega$
3. Note down  $I_L$  and  $V_L$  for each value of  $R_L$ . Where  $I_L$  and  $V_L$  are current through  $R_L$  and voltage across  $R_L$  respectively.
4. Prepare observation table showing readings of  $R_L$  Vs power  $P = I_L \cdot V_L$
5. Plot graph of  $P$  Vs  $R_L$
6. Locate the point of maximum value of power  $P$  and note down corresponding value of  $R_L$ .  
Verify the results theoretically

### Observation Table:

Sr. No.	$R_L\ \Omega$	Circuit Current ( $I_L$ ) in mA		Voltage ( $V_L$ ) in Volts	Power absorbed by load ( $P_L$ ) in W $P_L = I_L^2 \cdot R_L$	
		Theoretical	Practical		Theoretical	Practical
1.	100	0.0227	0.022	2.10	0.0515	0.0441
2.	200	0.0197	0.018	4.00	0.07761	0.080
3.	300	0.0174	0.016	5.16	0.0908	0.088
4.	400	0.0156	0.014	6.32	0.0973	0.099
5.	500	0.01415	0.014	7.09	0.1001	0.1005
6.	560	0.0133	0.012	7.52	0.1004	0.1009
7.	600	0.01293	0.012	7.78	0.08496	0.1008
8.	700	0.01190	0.010	8.26	0.09912	0.097
9.	800	0.01102	0.010	8.78	0.09715	0.096
10.	900	0.01027	0.010	9.20	0.0953	0.094
11.	1 K	0.00961	0.009	9.65	0.0924	0.093

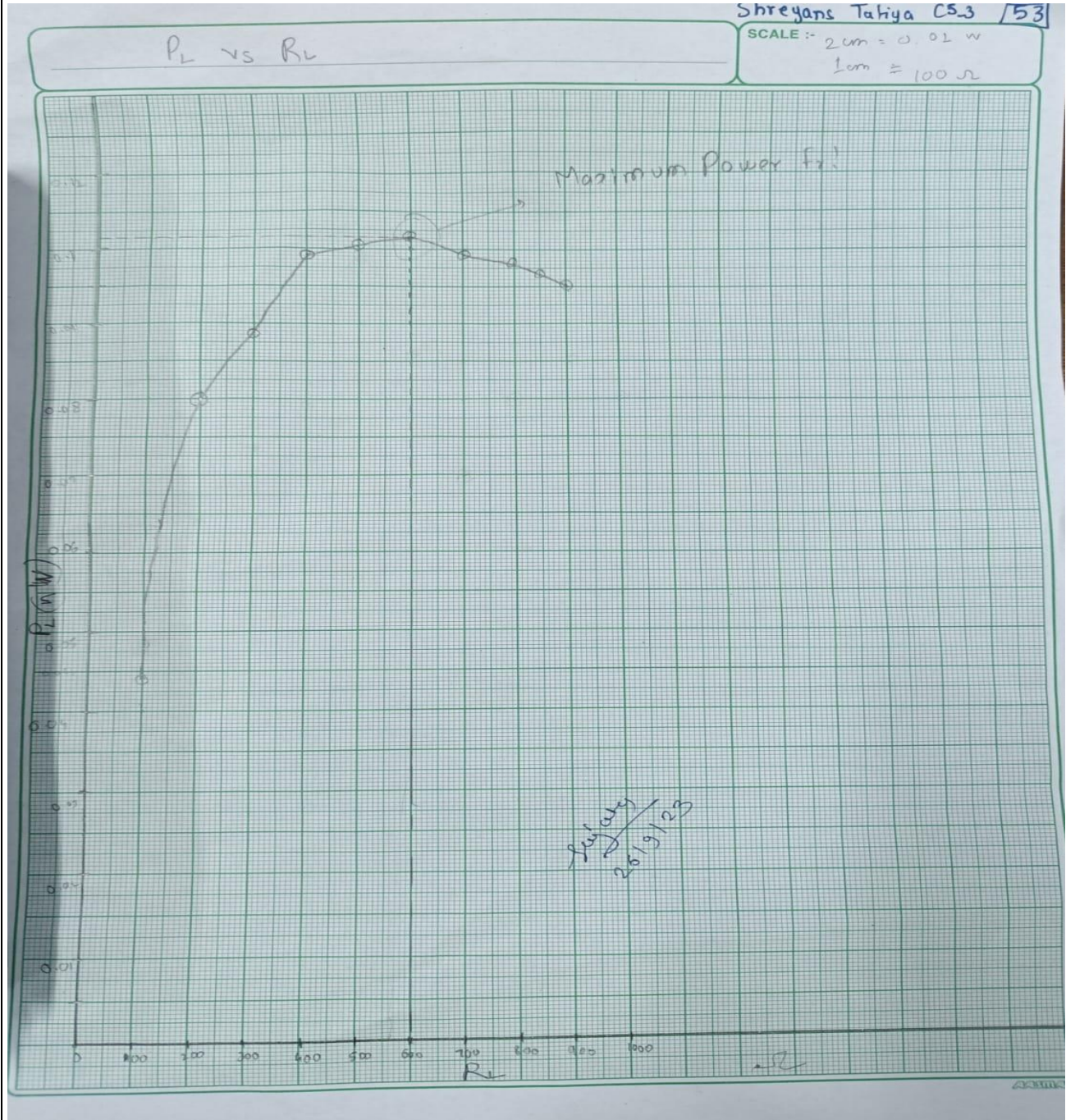**Graph:** Draw a graph showing effect of variation in  $R_L$  on  $P_L$  using observation table. Take  $R_L$  on X-axis and  $P_L$  on Y-axis. (Use a graph paper)



### Conclusion-

This theorem states that the maximum power that can be transferred from source to load is 50%, which occurs when source impedance is exactly matched to load impedance.

### Post-Lab Questions:


1. Explore one practical application where Maximum Power Transfer Theorem is used.

**Ans:**

The Maximum Power Transfer Theorem finds practical application in audio systems, where it helps optimize the matching of amplifier output impedance with speaker input impedance, ensuring efficient power transfer and high-quality sound reproduction.

2. Draw a block diagram or circuit diagram of this application.

**Ans:**

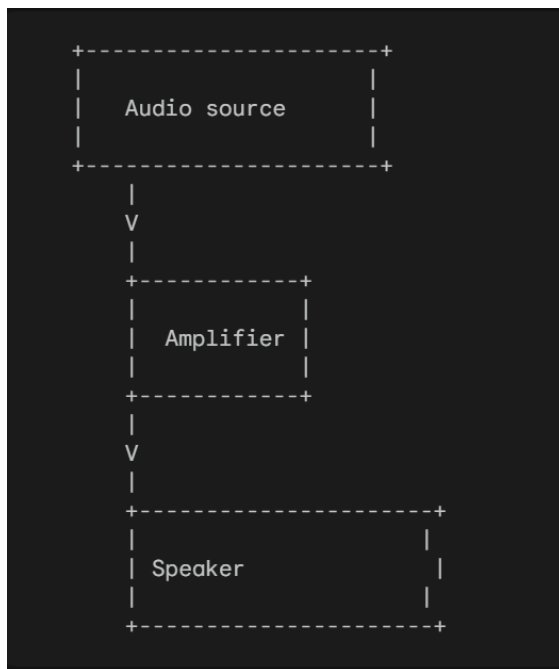

3. Explain in brief.

**Ans:** The Maximum Power Transfer Theorem is commonly applied in the design and analysis of electrical circuits, especially in the context of audio systems. For instance, in

audio amplifiers, the theorem helps optimize the matching of the output impedance of the amplifier with the input impedance of the speaker. When these impedances are well matched, the power transfer from the amplifier to the speaker is maximized, resulting in efficient energy utilization and improved audio quality. This application ensures that the electrical power generated by the amplifier is efficiently delivered to the speaker, producing clear and high-quality sound for various audio systems, including home theaters, music systems, and public address systems.

**OR**


**Answer the following:**

- 4. Do you apply Thevenin's Theorem to calculate Maximum Power across load resistor in a D.C. circuit?**

**Ans:** Yes, Thevenin's Theorem can be used to calculate the maximum power across a load resistor in a D.C. circuit.

- 5. Take a sample problem. Draw a block diagram or circuit diagram of this sample problem.**

**Ans:**

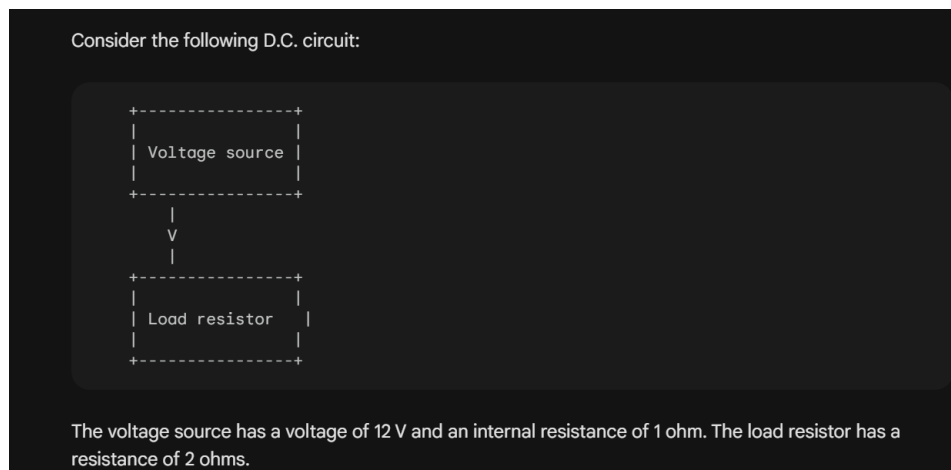




Block diagram:

Voltage source  $\rightarrow$  Load resistor

Circuit diagram:

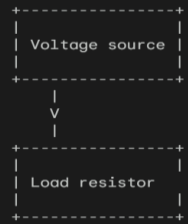

**6. Explain the solution in brief.**

**Ans:**

The maximum power transfer is achieved when the load resistance is equal to the Thevenin resistance. In this case, the load resistance is already equal to the Thevenin resistance. Therefore, the maximum power that can be dissipated across the load resistor in this circuit is 96 W.

**Signature of faculty in-charge with Date:**