

5/11/2023



**SOMAIYA**  
VIDYAVIHAR UNIVERSITY

Batch: C5-3 Roll No.: 16010123325


Name: Shreyans Tatiya

Course: EEEE - IA


Experiment / assignment / tutorial No. 1

Grade:  Signature of the Faculty with date

Q1]

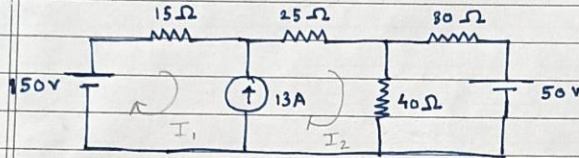

① Finding  $V_{TH}$

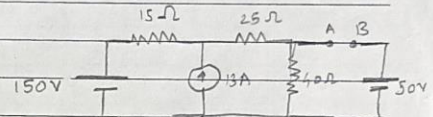

$$I_2 - I_1 = 13 \quad \text{--- ① [Supermesh]}$$

Using KVL in loop ① & ②,

$$150 - 15I_1 - 25I_2 - 40I_2 = 0$$

$$\therefore 15I_1 + 65I_2 = 150 \quad \text{--- ②}$$

Solving ① & ②,

$$\therefore I_1 = -8.6875 \text{ A}$$

$$I_2 = 4.3125 \text{ A}$$

Applying KVL in loop ③,

$$40I_2 - V_{TH} - 50 = 0$$

$$V_{TH} = 40I_2 - 50$$


$$V_{TH} = 122.5 \text{ V}$$

② Finding  $R_{TH}$


$$15 + 25 = 40 \Omega$$

$$\therefore (40 \parallel 40) = 20 \Omega$$

$$\therefore R_{TH} = 20 \Omega$$

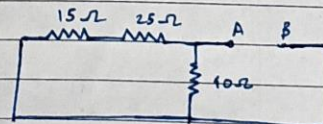

③ Finding  $I_L$

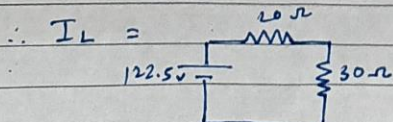


$$\therefore I_L = \frac{122.5}{20 + 30} = 2.45 \text{ A}$$

$$\therefore V_{TH} = 122.5 \text{ V}, \quad R_{TH} = 20 \Omega, \quad I_L = 2.45 \text{ A}$$

Simulate the circuit shown in figure 1, using LTspice software and measure  $V_{th}$ ,  $R_{th}$  and  $I_L$ . Tabulate the results as shown in the table below.

Parameter	Theoretical value	Simulated value
Thevenin's voltage $V_{th}$	122.5 V	122.5V
Thevenin's resistance $R_{th}$	20 $\Omega$	20 $\Omega$
Load current $I_L$	2.45 A	2.45 A

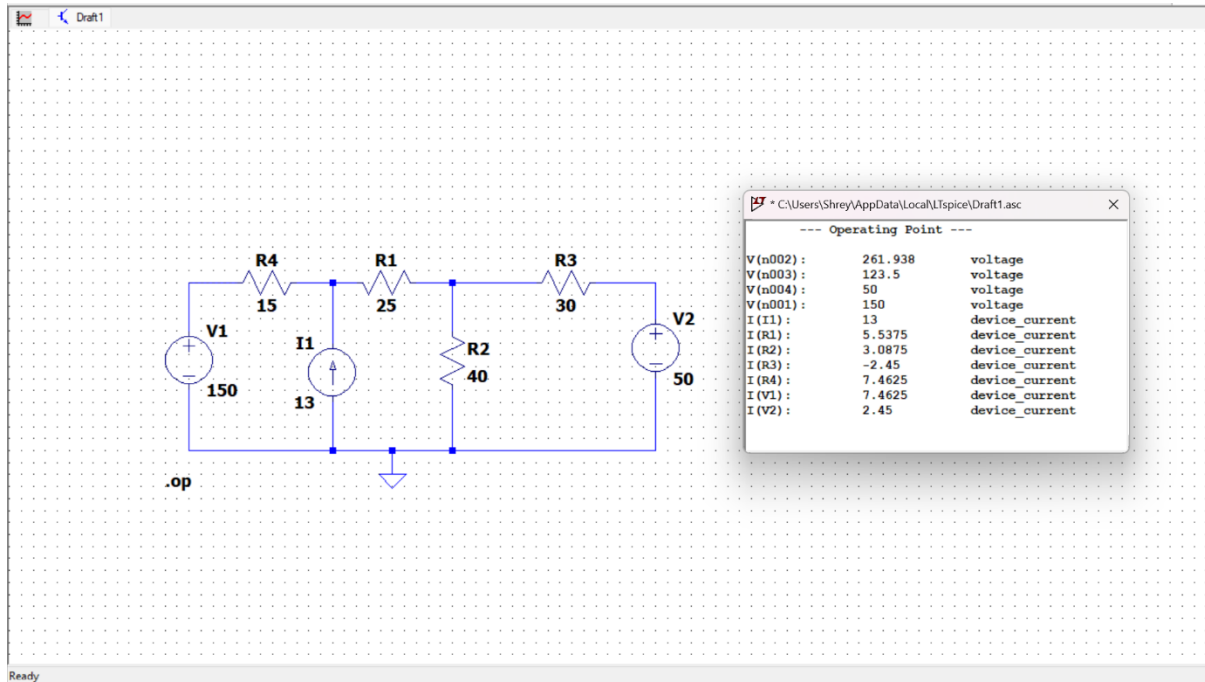

Q1 Shreyans Tatiya 16010123325

For Finding VTH  
 1) Remove Load RL  
 2) Measure VTH or V(ab)

.op

V(a): 172.5 voltage  
 V(b): 50 voltage  
 $V(ab) = VTH = V(a) - V(b) = 172.5 - 50 = 122.5$

--- Operating Point ---		
V(n002):	280.312	voltage
V(a):	172.5	voltage
V(n001):	150	voltage
V(b):	50	voltage
I(R1):	13	device_current
I(R2):	4.3125	device_current
I(R4):	4.3125	device_current
I(V1):	8.6875	device_current
I(V2):	0	device_current

Ready

Q1 Shreyans Tatiya 16010123325

For Finding RTH  
 1) Remove Load RL  
 2) Deactivate all sources

$Vx = 10V$   
 $Rth = Vx / I(Vx)$

.op

I(Vx): -0.5 device\_current  
 $Rth = 10 / 0.5 = 20 \text{ ohm}$

--- Operating Point ---		
V(n001):	-3.75	voltage
V(n002):	-10	voltage
I(R1):	0.25	device_current
I(R2):	-0.25	device_current
I(R4):	-0.25	device_current
I(V1):	-0.5	device_current

Ready

LTspice - [Draft1]

File Edit Hierarchy View Simulate Tools Window Help

Q1 Shreyans Tatiya 16010123325

VTH 122.5

RTH 20

Vx 0

RL 30

I(Vx): 2.45 device\_current

--- Operating Point ---

V(n001):	-3.75	voltage
V(n002):	-10	voltage
V(n003):	122.5	voltage
V(n005):	73.5	voltage
V(n004):	73.5	voltage
I(R1):	0.25	device_current
I(R2):	-0.25	device_current
I(R4):	-0.25	device_current
I(R1):	-2.45	device_current
I(Rth):	-2.45	device_current
I(V1):	-0.5	device_current
I(Vth):	-2.45	device_current
I(Vx):	2.45	device_current

Ready



5/11/2023



**SOMAIYA**  
VIDYAVIHAR UNIVERSITY

Batch: <u>CS-3</u>	Roll No.: <u>16010123325</u>
Name: <u>SHREYANS TATIYA</u>	
Course: <u>EEEE-IA</u>	
Experiment / assignment / tutorial No. <u>1</u>	
Grade: <input type="text"/>	Signature of the Faculty with date

Q4] Explain the principle and working of the Energy Meter with a neat labelled diagram.

Principle:

→ A single phase Energy meter is used for measuring the power consumed in Kilowatt-hours (KWh) of a domestic or industrial electrical installation.

On a single phase AC supply, the electromechanical induction by counting the revolutions of a non-magnetic, but electricity conductive, metal disc which is made to rotate at a speed proportional to the power passing through the meter

Construction:

→ A single phase energy meter is a sort of induction type watt-hour meter. It consists of two electromagnets. When the meter is connected to the supply line and the load, then both the coils produce their magnetic fields. The field produced by the circuit coils directly proportional to the magnitude of the current flowing through it. The field produced by the pressure coil depends on the voltage across it. Both the fluxes producing and two eddy currents and therefore two driving, torques resultant produced on the disc.

The damping torque is produced by the permanent magnet. Shading rings are mounted on the shunt magnet for the correction in power factor of the meter. The rotational speed of the disc is counted by a counting mechanisms which may be of any-one of the types (Cycloidal, clock dial, number dial).

Diagram

