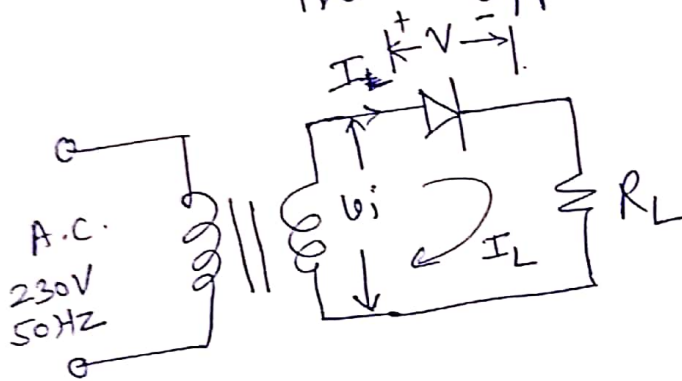


## Rectifiers.

→ Used in D.C. power supply  
A.C. to D.C.

### H.W. Rectifier

Rectifier → Device giving low resistance to current in one direction but a high resistance to current in opposite direction.





current through diode,

$$I = I_0 \left( e^{\frac{V}{\eta V_T}} - 1 \right)$$

where  $\eta = 1$  for Ge & 2 for Si.

$$V_T = \frac{T}{11,600}$$

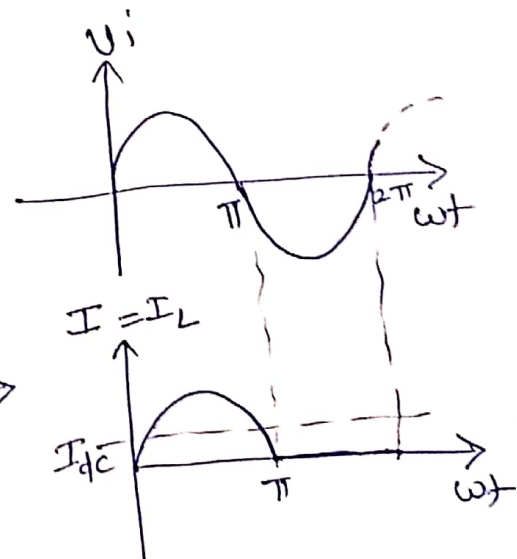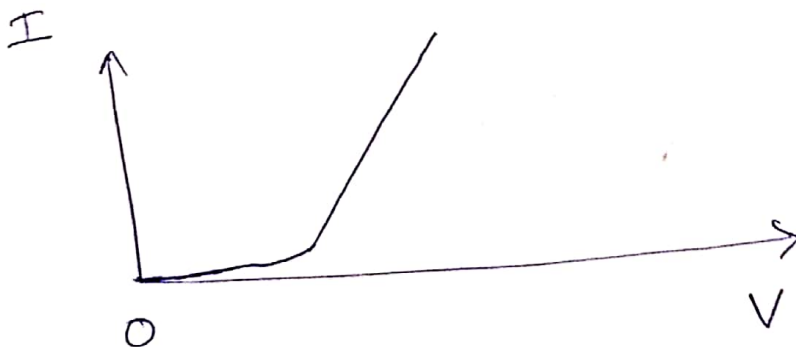

① Reading of d.c. Ammeter

$$I_{d.c.} = \frac{I_m}{\pi}$$

② Reading of A.C. Ammeter.

$$I_{rms} = \frac{I_m}{2}$$

③  $V_{d.c.} = \frac{I_m}{\pi} \cdot R_L$

④ ripple factor = measure of fluctuating current.

$$r = \frac{\text{rms. value of A.C. component of wave}}{\text{Average value.}}$$



$$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

$$r = \sqrt{\left(\frac{I_m/2}{I_m/\pi}\right)^2 - 1} = 1.21$$

Meaning - A.C. component is more than D.C. component.

→ Poor Rectifier.



H.W. with capacitor.

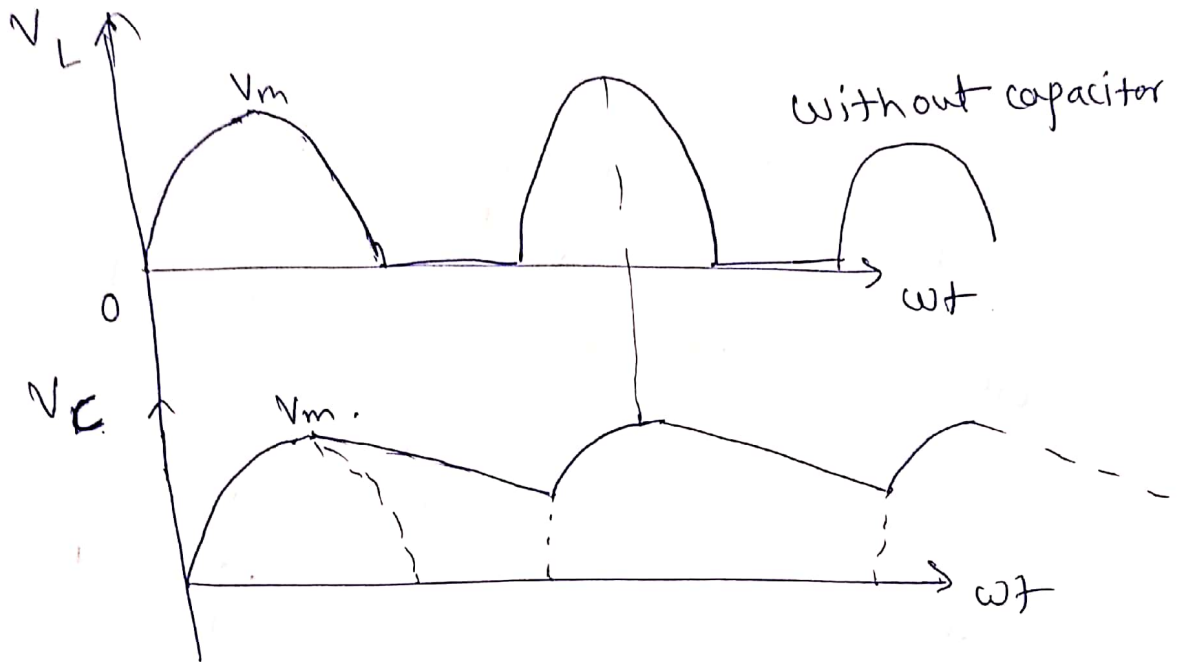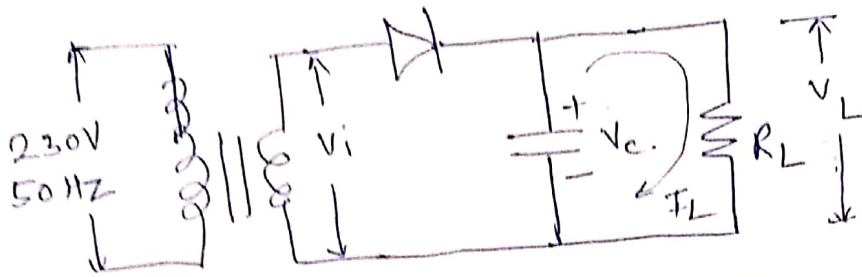



$I_L$  flows when  $V_c \geq V_m$ .

$$\text{Ripple factor } r = \frac{2}{2fR_LC - 1}$$

# F. W. with resistive Load.

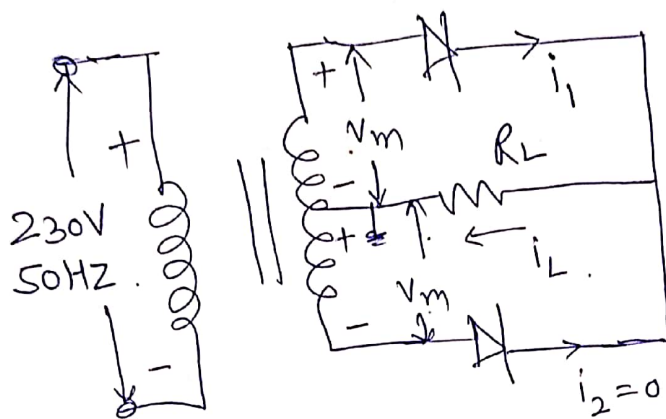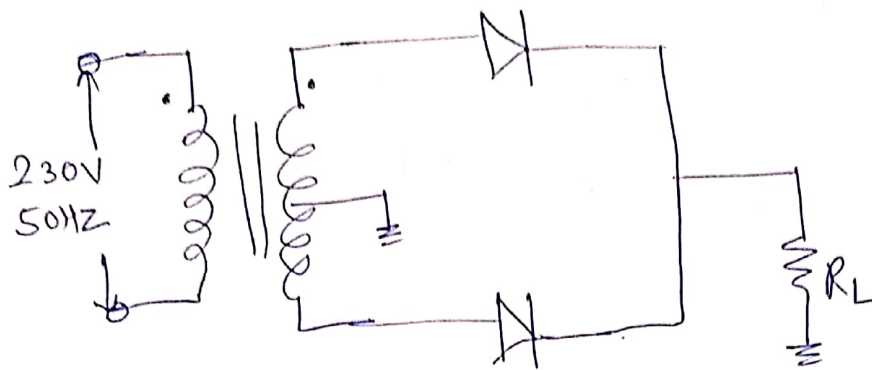

+ve cycle (Half)


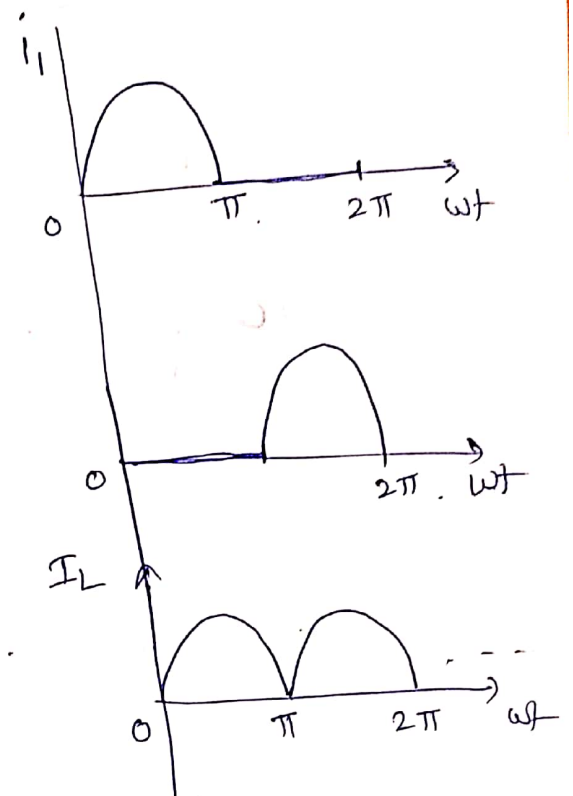
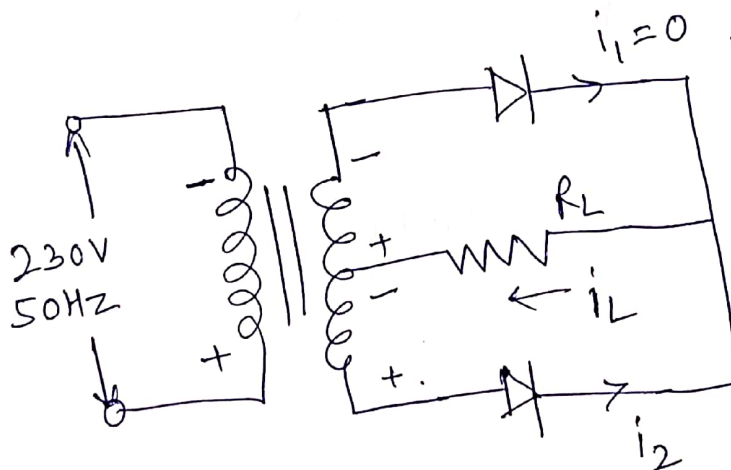


$$(1) I_{dc} = \frac{2I_m}{\pi}$$

$$(2) I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$(3) \text{ ripple factor } r = \frac{I_{rms}}{I_{dc}} = \frac{I_m/\sqrt{2}}{2I_m/\pi} = 1.11$$
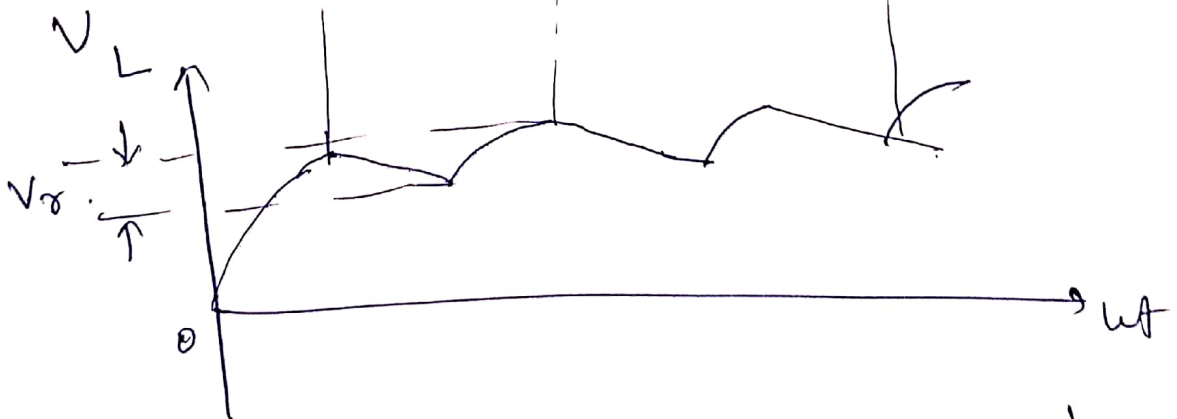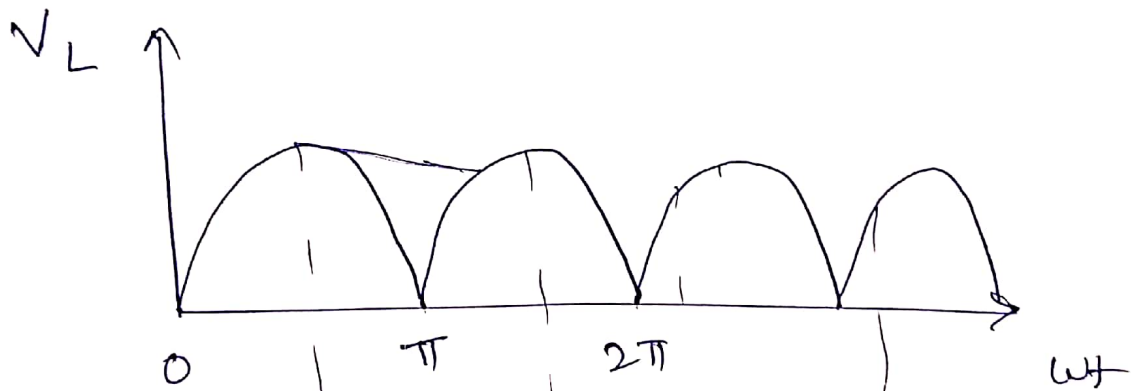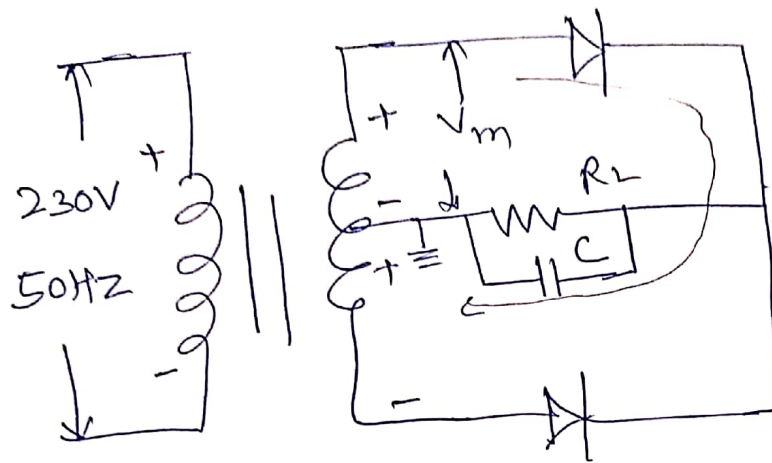
# Full wave rectifier with capacitor filter.



$$r = \frac{1}{4\sqrt{3} f C R_L} \quad \therefore r \propto \frac{1}{R_L}$$

$$\& \quad r \propto \frac{1}{C}$$

Useful for light load.